

(Following Paper ID and Roll No. to be filled in your Answer Book)

PAPER ID : 3302

Roll No.

--	--	--	--	--	--	--	--	--	--

B.Tech.

(SEM II) EVEN SEMESTER THEORY EXAMINATION, 2009-2010

ELECTRONICS ENGINEERING

Time : 3 Hours

Total Marks : 100

Note : Attempt ALL questions.**SECTION - A**

Attempt all parts of this question. All parts of the question carry equal marks.

1. This question contains 10 objective type/fill in the blank type/true-false type questions. Select most appropriate option. (10x2=20)
- (a) When we apply reverse bias to a junction diode, it :
- (i) lowers the potential barrier.
 - (ii) raises the potential barrier.
 - (iii) greatly decreases the minority-carrier current.
 - (iv) greatly increases the majority-carrier current.
- (b) Ripple frequency of the output wave form of a full-wave rectifier when fed with a 50 Hz sine wave is :
- (i) 25 Hz
 - (ii) 50 Hz
 - (iii) 100 Hz
 - (iv) 200 Hz
- (c) "An ordinary transistor is called 'Bipolar Junction Transistor' because it has two poles-one positive and the other negative". The statement is :
- (i) True
 - (ii) False

- (d) The transistor configuration which provides highest output impedance is :
- Common Base
 - Common Emitter
 - Common Collector
 - None of the above
- (e) In a Field Effect Transistor (FET) the gate to source voltage that gives zero drain current is called _____ voltage.
- (f) When the positive voltage on the gate of a p-channel JFET is increased, its drain current :
- increases
 - decreases
 - remains the same
 - none of the above
- (g) For the circuit shown in Figure - 1., the output voltage v_o is given by :

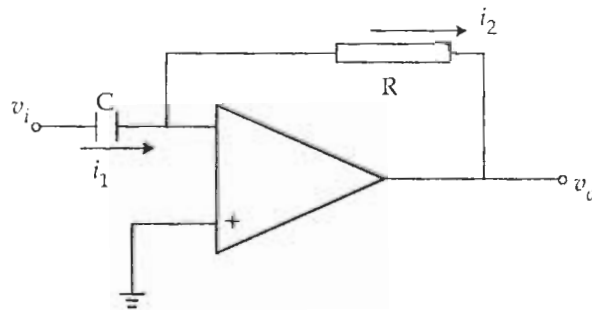


Figure - 1

- $v_o = -\frac{1}{RC} \frac{dv_i(t)}{dt}$
- $v_o = -\frac{1}{RC} \int_0^t v_i(t) dt$
- $v_o = -RC \frac{dv_i(t)}{dt}$
- $v_o = -RC \int_0^t v_i(t) dt$

- (h) Three Boolean operators are :
- (i) NOT, OR, AND
 - (ii) NOT, NAND, OR
 - (iii) NOR, OR, NOT
 - (iv) NOR, NAND, NOT
- (i) Lissajous pattern obtained on the screen of a CRO can be used to determine :
- (i) Phase shift
 - (ii) Amplitude distortion
 - (iii) Voltage amplitude
 - (iv) None of the above
- (j) "A digital voltmeter has negligible loading effect on the circuit under test because its input resistance is very high". The above statement is :
- (i) True
 - (ii) False

SECTION - B

2. Attempt *any three* parts of the following : (3×10=30)
- (a) (i) Describe the conditions established by forward and reverse-bias conditions on a p-n junction diode and how the resulting current is affected.
 - (ii) Calculate forward current I_F for the silicon diode with dynamic resistance $r_d = 0.25\Omega$ used in the following circuit of Figure - 2.

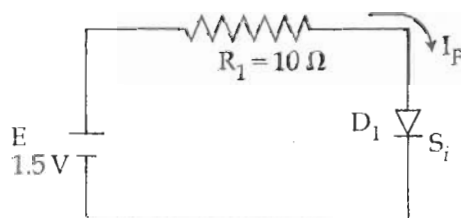


Figure - 2

- (b) (i) What is the major difference between a bipolar and an unipolar device ? Explain with example.
- (ii) Draw and explain the input and output characteristics of common base configuration using npn bipolar junction transistor. Indicate all the region of operations.
- (c) (i) What are the advantage of FET over BJT. Explain.
- (ii) Derive expressions for voltage gain of inverting and non-inverting ideal operational amplifier configurations.
- (d) (i) What are universal gates ? Why they are called so ? Justify your answer.
- (ii) What do you understand by don't care conditions ? Is it an advantage or disadvantage to include them in a map. Explain with reasons.
- (e) Draw the block diagram of a CRO and briefly explain the function of each block.

SECTION - C

Attempt all questions. All questions carry equal marks.

(5x10=50)

3. Attempt *any two* parts of the following :

(2x5=10)

- (a) Describe the physical mechanism of Zener breakdown. For the circuit shown in Figure-3, find the voltage drop across the $5\text{ k}\Omega$ resistance.

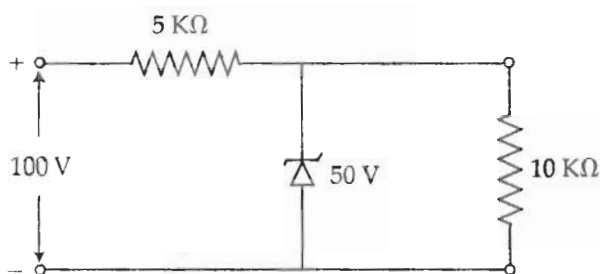


Figure - 3

- (b) Sketch a two - diode full wave rectifier circuit for producing a positive output voltage. Sketch the input and output waveforms and explain the circuit operation.
- (c) Draw a voltage doubler circuit. Sketch input and output waveforms and explain the circuit operation.

4. Attempt *any one* of the following :

(1×10=10)

- (a) Derive the expressions for voltage gain, current gain and input impedance in terms of h-parameters for common emitter amplifier.
- (b) Determine the following for the voltage divider bias circuit shown in Figure-4.
- (i) I_C (ii) V_E (iii) V_B (iv) V_{CE} and (v) R_i

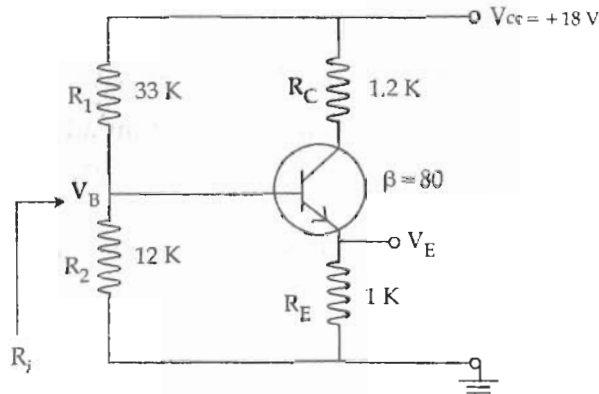


Figure - 4

5. Attempt *any one* of the following :

(1×10=10)

- (a) Describe the construction and operation of a MOSFET in enhancement mode. Draw its characteristics and equivalent circuit of the device.
- (b) (i) Draw the circuit diagram for unity gain amplifier. Where is it used and why ?
- (ii) Find the output voltage of the following op-amp circuit shown in Figure-5.

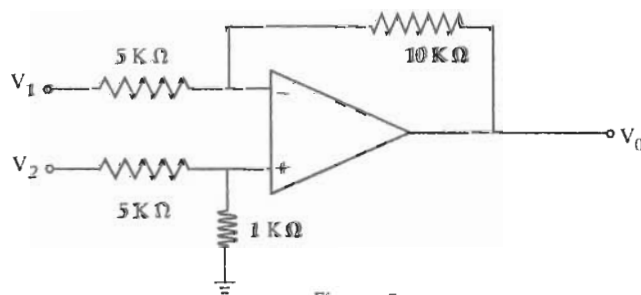


Figure - 5

6. Attempt *any two* parts of the following : (2x5=10)

(a) (i) Add and subtract without converting the following two octal numbers 7461 and 3465.

(ii) Convert the following numbers as indicated :

(A) $(62.7)_8 = (\text{_____})_{16}$

(B) $(BC\ 64)_{16} = (\text{_____})_{10}$

(C) $(111011)_2 = (\text{_____})_5$

(b) (i) Represent the unsigned decimal number 965 and 672 in BCD and then show the steps necessary to form their sum.

(ii) Express the Boolean function $F = xy + z$ in a product of max term form.

(c) Given the Boolean function.

$$F(A, B, C, D) =$$

$$\bar{A} \bar{B} \bar{C} + A \bar{C} \bar{D} + A \bar{B} + A B C \bar{D} + \bar{A} \bar{B} C$$

(i) Express it in sum of minterms.

(ii) Find the minimal sum of products expression using K-map and implement the output using NAND gates only.

7. Attempt *any one* of the following : (1x10=10)

(a) Draw the Lissajous pattern you expect when the ratio of the frequency of the vertical input to that of the horizontal input is 1 : 2. Explain with the help of a neat diagram, why you get this pattern.

(b) Explain briefly the working principle of a digital voltmeter. What are the advantages obtained by numeric read out ?

- o o o -